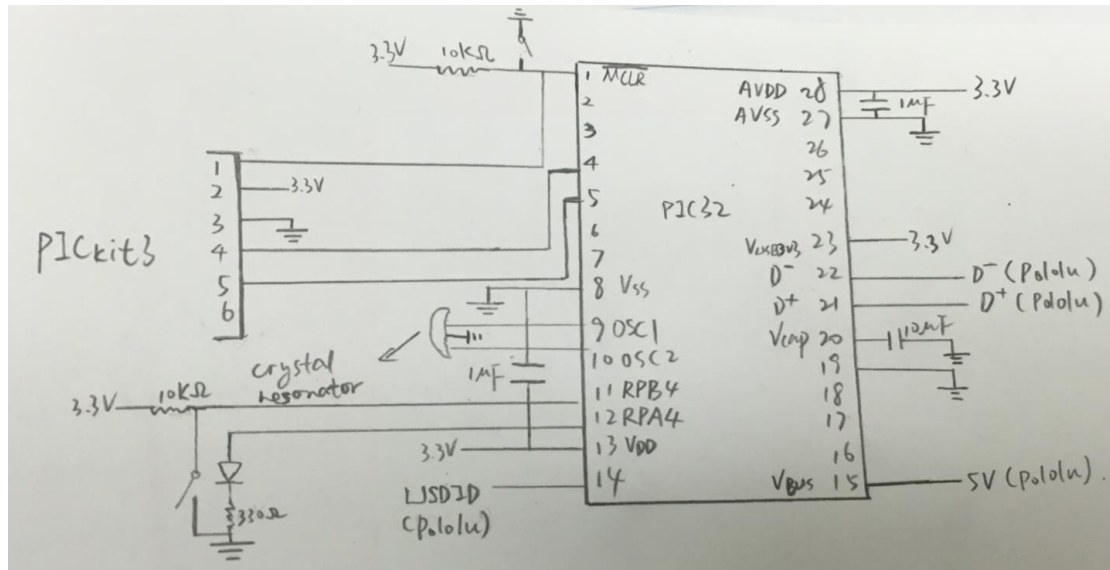



1.

1.




2.

3.3V with oscillations:

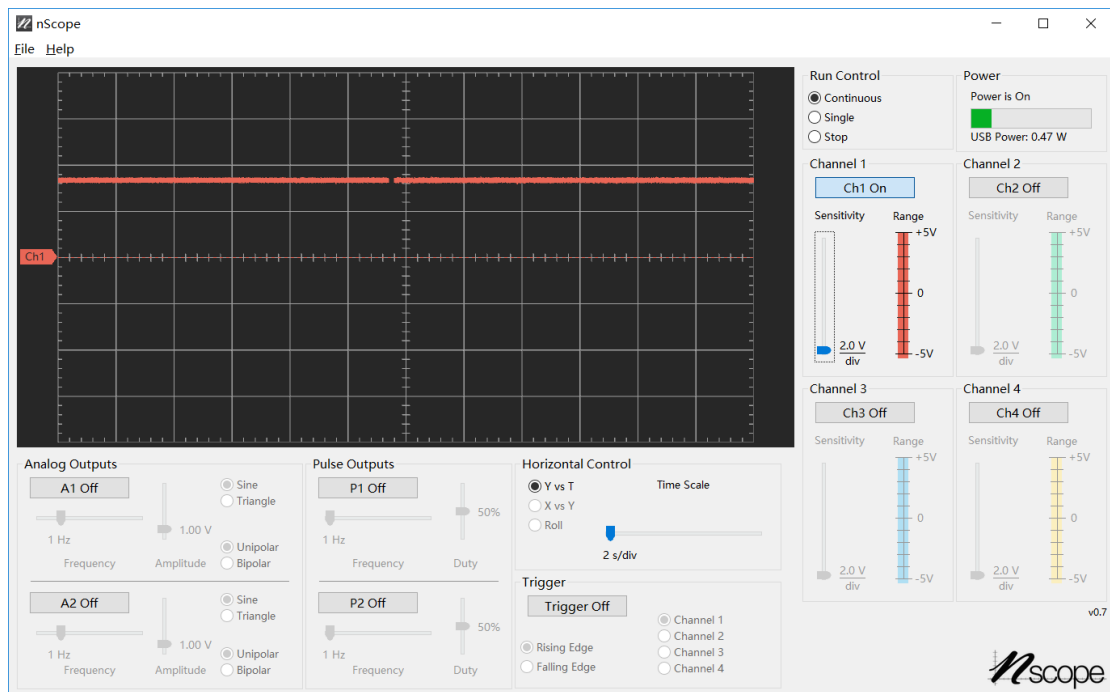

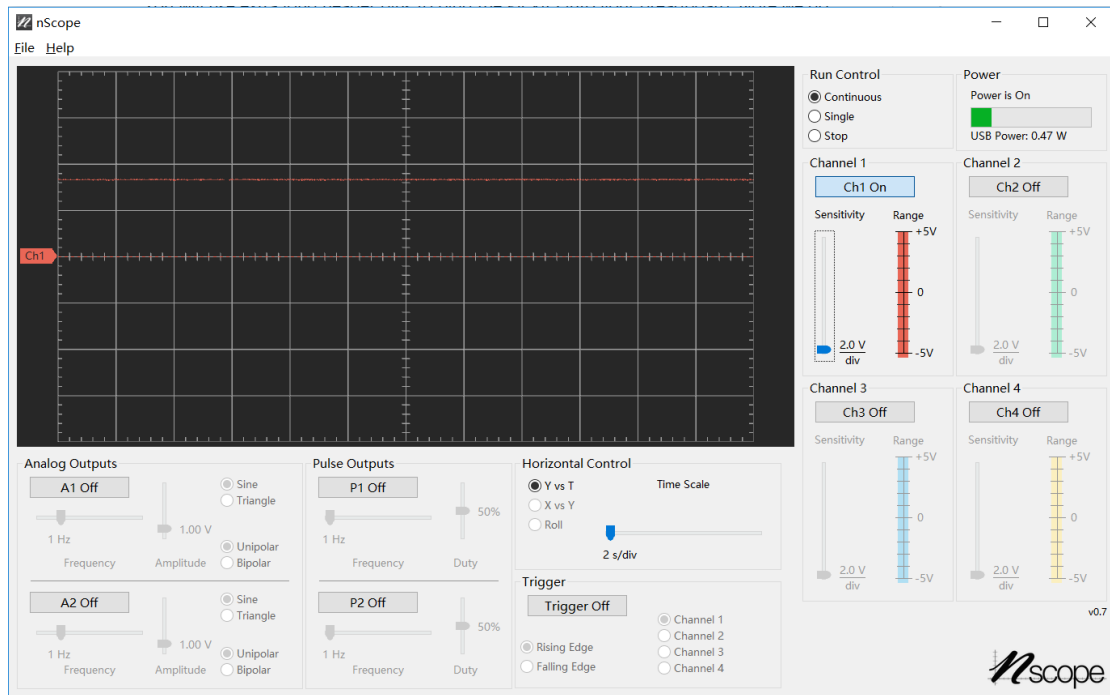Clean 3.3V: (when add the output 1uF capacitor, the oscillations go away)



6.

